

ZDC Semilab Summer Workshop



Project Task: UART Transmitter Module

Presented by: ZDC Team



Date: 2/8/2024

Welcome to the ZDC Semilab Summer Workshop! This project task involves the design and implementation of a UART transmitter. You will explore the fundamentals of serial communication and gain hands-on experience in digital IC design.

Project Overview:

- **Objective:** To design a functional UART transmitter module.
- **Learning Outcomes:** Understanding of serial communication, hardware design, and implementation.

  - **UART** stands for Universal Asynchronous Receiver / Transmitter
- **Definition:** UART is a hardware communication protocol used for asynchronous **serial** communication between devices.
- **Asynchronous Communication:** No common clock signal; data is synchronized using start and stop bits.




What is the difference between serial and parallel communication ?

Comparison	Serial	Parallel
Bit / Cycle	Only one Bit / Cycle	Multiple Bits / Cycle
Speed	Typically, slower	Typically , faster
Hardware Complexity	Low	High
Disadvantages	Typically, Lower throughput	<ul style="list-style-type: none"> - Affected by clock Skew - Wires length is limited due to cross talk


Although serial protocols use a single channel, they may be preferred in certain applications due to their simplicity and the potential to achieve higher clock frequencies compared to parallel protocols

Noted that : the choice depends on specific application requirements

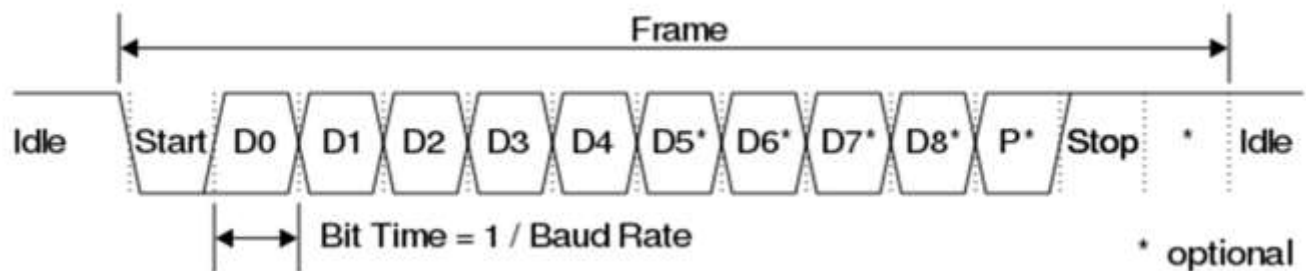Data Format: Typically, 8 data bits, 1 start bit, (1 or 2) stop bits, and optional parity bit.




Transmitter Operation :

 

- When idle, the transmitter send a stream of ones.
- The start bit is 0.
- The data length can either be 7 or 8.
- The parity bit is optional and can either be odd or even.
- • The stop bit/s can be 1 or 2.

Basic Transmitter Architecture :

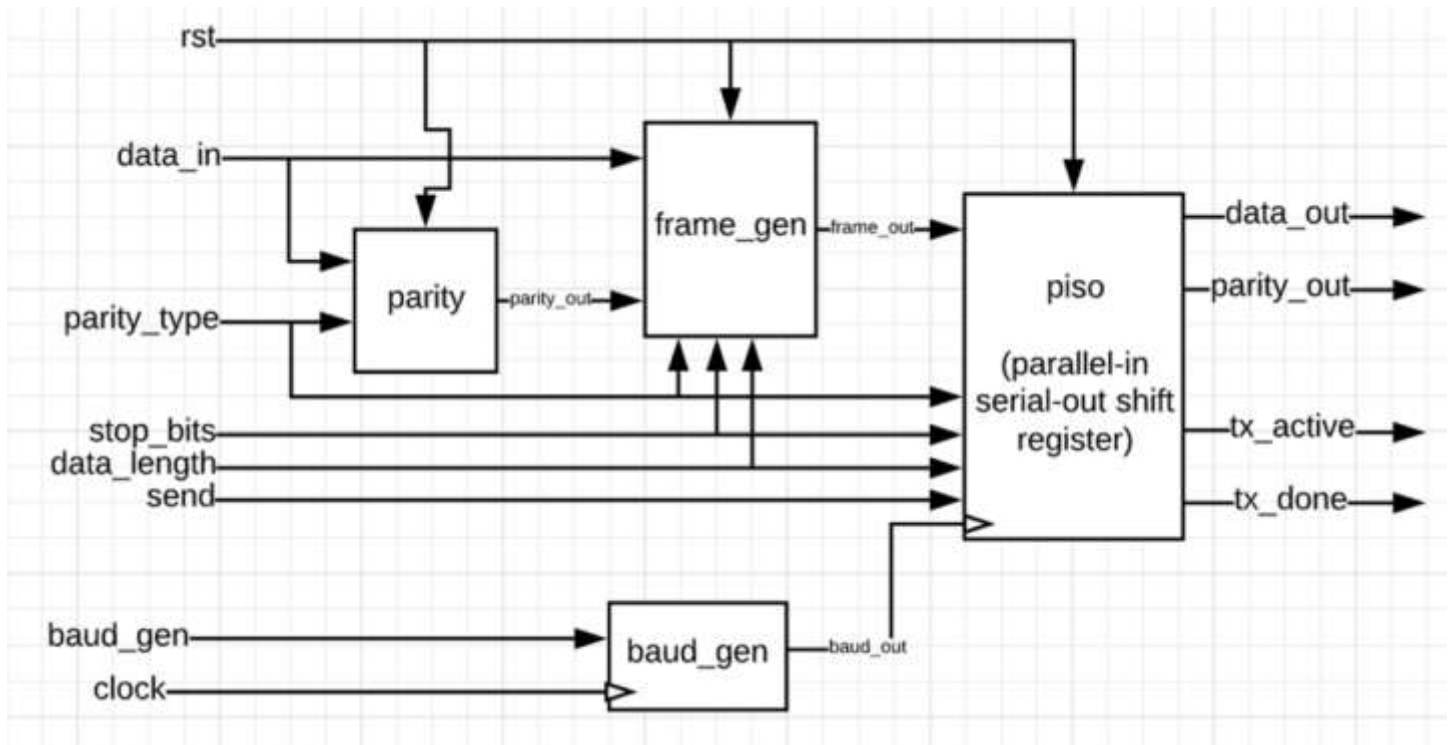

Component :

1) Parity Detector

- A parity bit is a basic method to check whether the received data is correct
- It can be either even parity or odd parity.
- With even parity, the bit is only 0 when the number of ones is even.
- With odd parity, the bit is only 0 when the number of ones is odd.

Parity type signal:

if 00 no parity , (parity will not exist in fram) .


if 01 odd parity.

if 10 even parity.

if 11 use the output “**parity_out**” as an **odd parity** bit and no parity in the serial frame(like 00).

 2) Frame Generator

- receives **data_in** may be 7 or 8 bits in **parallel**
- Receives parity bit “Parity_out” , may not accept it in case of parity_type “00” , “11”
- Receives **stop_bits** :
if **low** : One stop bit in the frame
If **High**: Two stop bits in the frame
- Receives **data_length**
if **low** : 7 bits in the frame.
If **High**: 8 bits in the frame.



3) Parallel in Serial out “PISO”

- Receives the full frame in **parallel** and convert it to **serial** respectively at **data_out**
- The frame is transmitted when “**Send**” is asserted
- As long as the frame is still transmitted , signal “**tx_active**” is asserted
- Once the frame (i.e. start , data , parity , stop) is completed regardless of frame length, Signal “**tx_done**” is asserted
- Signal “**parity_out**” is asserted only when signal “**parity_type**” = 11 as previously mentioned

4) Baud Generator

- Baud rate is the number of serial bits per second(**Bits/Sec**) that can be transmitted/received over a certain communication line
- It receives **baud_gen** :
 - if 00 , 2400 baud (**Bits/Sec**)
 - If 01 , 4800 baud (**Bits/Sec**)
 - If 10 , 9600 baud (**Bits/Sec**)
 - If 11 , 19.2K baud (**Bits/Sec**)
- Assume the system **clock** frequency, for frequency division, is 50MHz.
- **Baud_out** is directly connected to **PISO** as a clock input

Notes :

- 1) You can use any microarchitecture as long as you will verify the specifications mentioned.
- 2) In the top file , Use **only** the port names specified in the given architecture and do not add any other signals .

You can use this for the top file :

```
module uart_tx(  
    //DO NOT EDIT any part of this port declaration  
    input          clock, rst, send,  
    input [1:0]    baud_rate,  
    input [7:0]    data_in,  
    input [1:0]    parity_type, //refer to the block comment above.  
    input          stop_bits,          //low when using 1 stop bit, high when using two stop bits  
    input          data_length,        //low when using 7 data bits, high when using 8.  
    output reg     data_out,            //Serial data_out  
    output reg     p_parity_out,        //parallel odd parity output, low when using the frame parity.  
    output reg     tx_active,           //high when Tx is transmitting, low when idle.  
    output reg     tx_done              //high when transmission is done, low when not.  
);
```

- 3) You must insert both RTL “code , schematic” and the simulation “Testbench”.

Don't be shy to ask for help.
